


How to power the Raspberry Pi Pico

Powering the Raspberry Pi Pico

The easiest way to power a Pico is through the USB cable either to a computer or a phone charger. If you are going for a wireless design, you can use batteries as well. This tutorial will demonstrate how to power a Pico with a 9V battery or 3 AA batteries.

Raspberry Pi Pico pinout

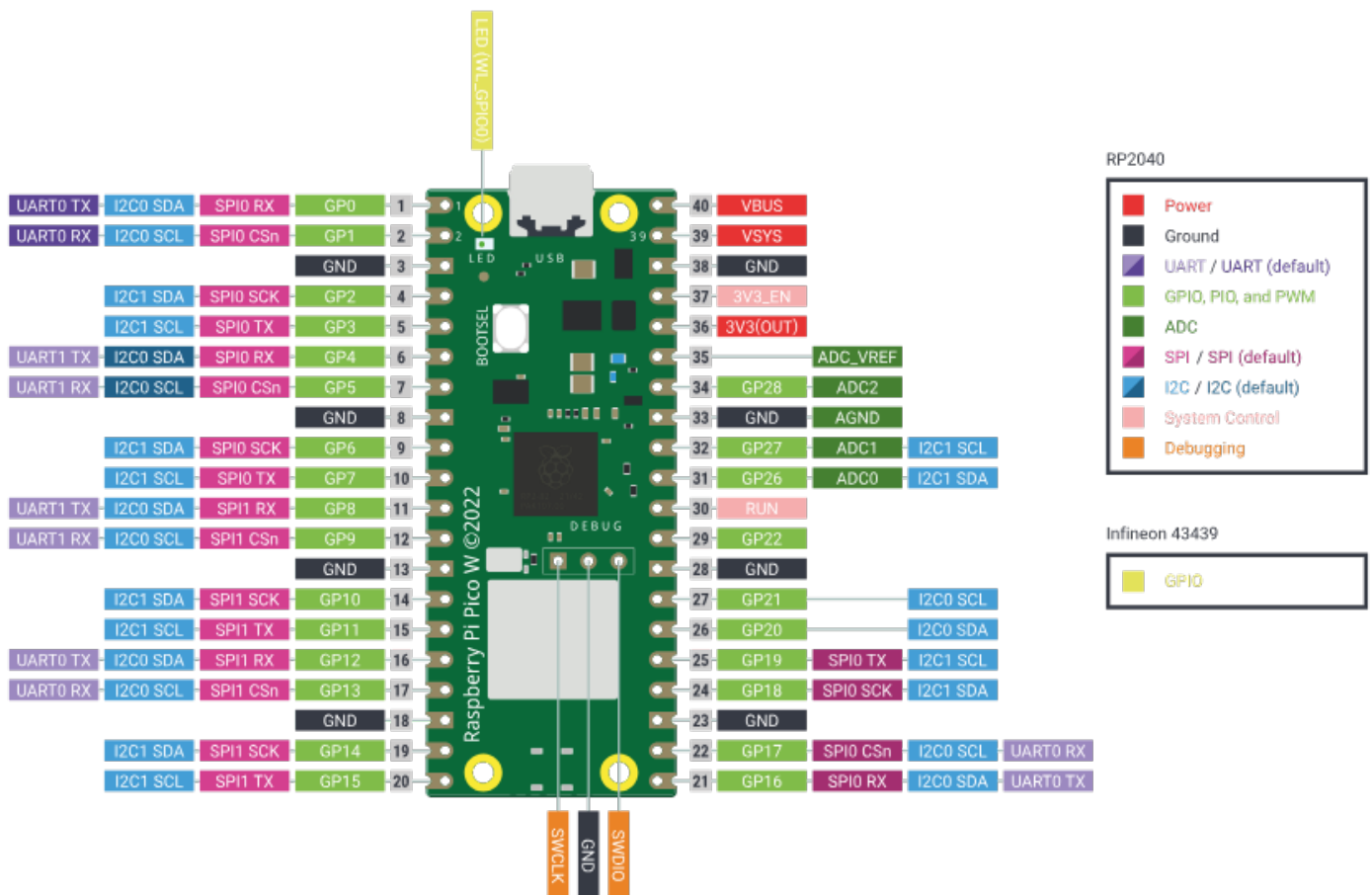You have to find out the pinout of the model you are using. The pins you are looking for are `VSYS` and `GND`. In this tutorial, a Pico W is used.



Raspberry Pi Pico's Power Need


`VSYS` (PIN 39): Pin for main system input voltage. The input voltage can vary between **1.8V to 5.5V**. This voltage is used by the onboard SMPS to generate 3.3V to power the RP2040 microcontroller and GPIOs.

Why these parts are needed

- **Switch:** When we are using batteries to power the microcontroller, a switch is preferred. Some battery holder has a built-in switch which will be more convenient for you. With a switch, you can turn off the Pico when not in use and not drain the battery.
- **LM7805:** The LM7805 is a popular voltage regulator integrated circuit (IC). It is a positive voltage regulator that provides a stable and fixed output voltage of +5 volts. It is widely used in electronic circuits to regulate the voltage and ensure a consistent and reliable power supply. It can accept an input voltage in the range of 7V to 35V, depending on the specific model, so you will need this when you are using a power supply with a voltage higher than 5V.
- **Diode:** - A diode is a semiconductor device that allows current to flow in one direction while blocking it in the opposite direction. In other words, it acts as a one-way valve for electric current. We need a diode for safety to prevent one power source from back-feeding the other. Raspberry Pi can have two power sources at the same time and there is a risk of unwanted power flow between the two power sources. Schottky diode is preferred for its low voltage drop, but any others should work with a bit of voltage drop around 0.2-0.6V.


9V battery

Part needed: switch, LM7805 & Any diode

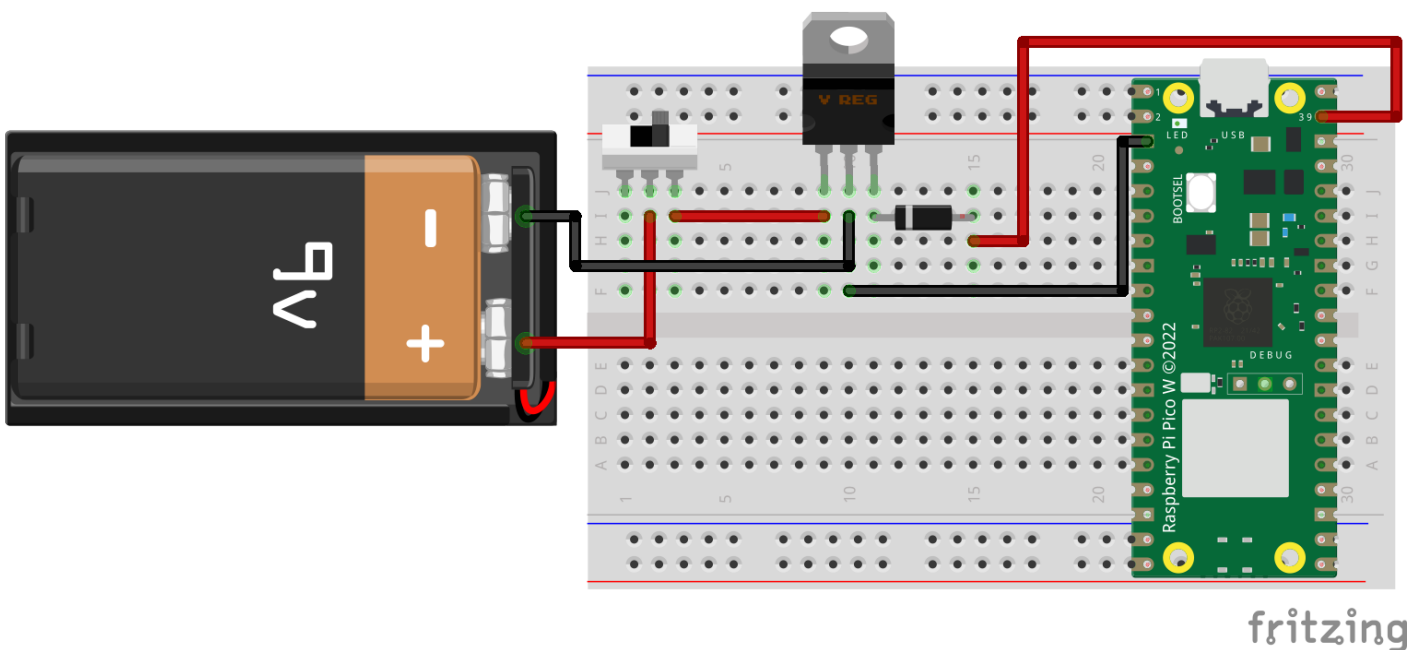

3 AA batteries

Part needed: switch & Any diode

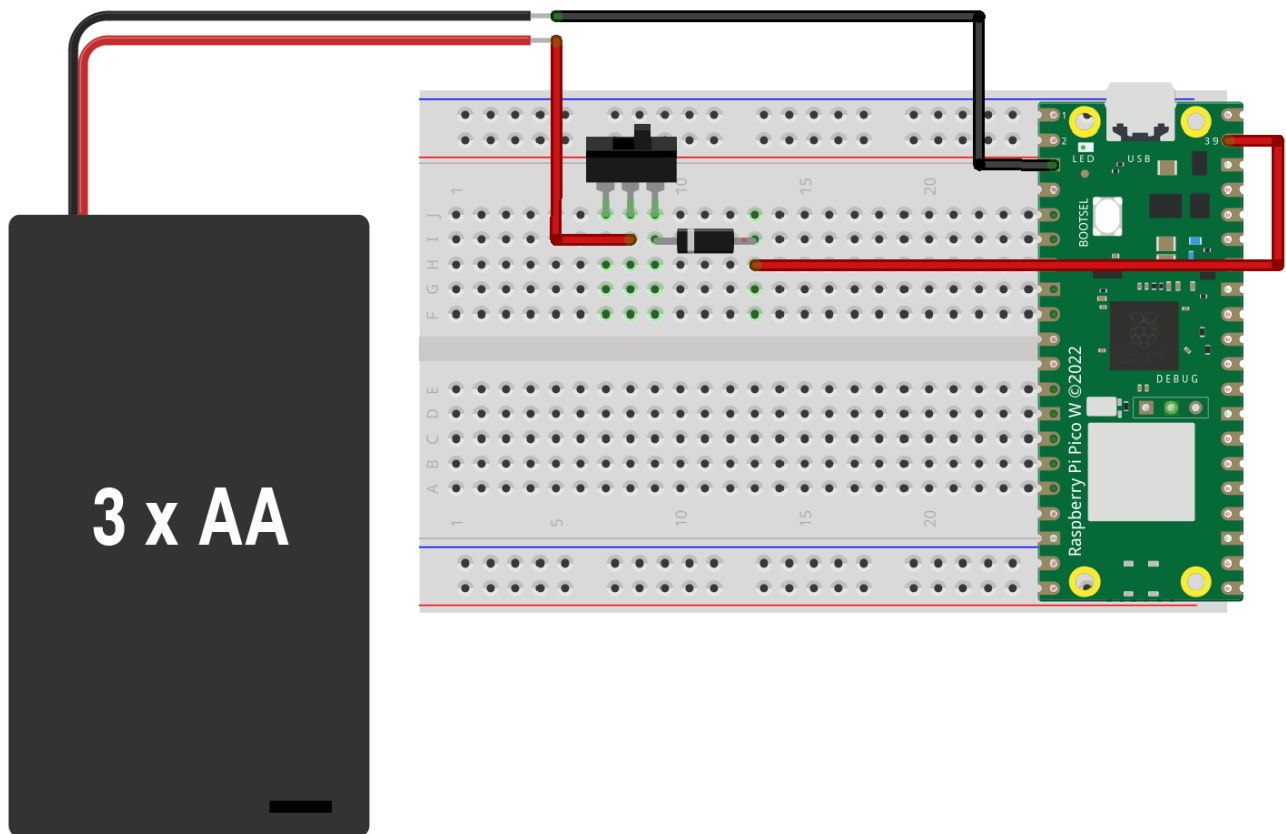

fritzing

Revision #4

Created 21 February 2024 14:56:44 by Joanne Leung

Updated 23 February 2024 12:30:59 by Joanne Leung